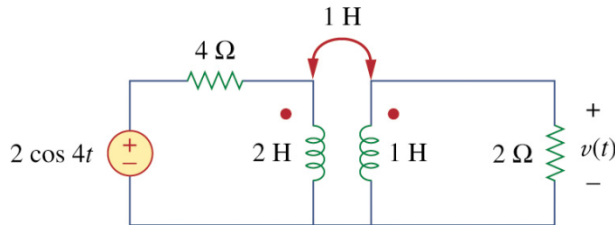


**This is the last homework assignment. Some of the content will require the lectures of December 4.**

**1:**

Find  $v(t)$  for the circuit below.



Let's use meshes, clockwise mesh current in both meshes,  $\mathbf{i}_1$  on the left,  $\mathbf{i}_2$  on the right.  $\omega = 4$ ,  $\mathbf{Z}_1 = j(4\text{r/s})(2\text{H}) = j8\Omega$ .  $\mathbf{Z}_2 = j(4\text{r/s})(1\text{H}) = j4\Omega$ .

$$\mathbf{Z}_M = j(4\text{r/s})(1\text{H}) = j4\Omega$$

KVL around left mesh

$$-2\angle 0^\circ + 4\mathbf{i}_1 + j8\mathbf{i}_1 - j4\mathbf{i}_2 = 0$$

$$(4 + j8)\mathbf{i}_1 - j4\mathbf{i}_2 = 2 + j0$$

KVL around right mesh

$$j4\mathbf{i}_2 + 2\mathbf{i}_2 - j4\mathbf{i}_1 = 0$$

$$-j4\mathbf{i}_1 + (2 + j4)\mathbf{i}_2 = 0$$

$$\begin{bmatrix} 4 + j8 & -j4 \\ -j4 & (2 + j4) \end{bmatrix} \begin{bmatrix} \mathbf{i}_1 \\ \mathbf{i}_2 \end{bmatrix} = \begin{bmatrix} 2 + j0 \\ 0 \end{bmatrix}$$


$$\begin{bmatrix} \mathbf{i}_1 \\ \mathbf{i}_2 \end{bmatrix} = \begin{bmatrix} 0.2059 + j0.1765 \\ 0.2353 - j0.0588 \end{bmatrix}$$

$$v = 2\mathbf{i}_2 = 0.47 - j0.12 = 0.485\angle -14^\circ$$

$$v(t) = 0.481\cos(4t - 14^\circ)$$

**2:**

Solve for  $v(t)$  in the circuit below

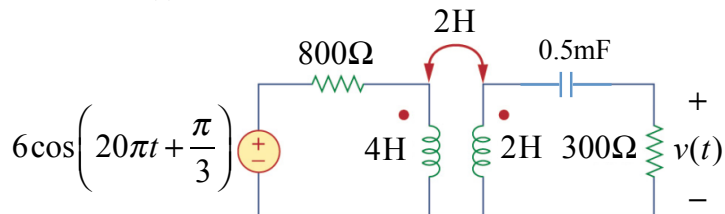

$$\mathbf{V} = 6\angle\frac{\pi}{3} = 6\angle 60^\circ = 3.0000 + j5.1962, \omega = 20\pi = 62.83\text{rad/sec}$$

$$\mathbf{Z}_N = j\omega 2\text{H} = j125.7\Omega$$

$$\mathbf{Z}_1 = j\omega 4\text{H} = j251.3\Omega$$

$$\mathbf{Z}_2 = j\omega 2\text{H} = j125.7\Omega$$

$$\mathbf{Z}_3 = \frac{1}{j\omega(0.5 \times 10^{-3}\text{F})} = -j31.83\Omega$$

Define clockwise mesh currents

In left hand mesh

$$-6\angle 60^\circ + 800\mathbf{I}_1 + j251.3\mathbf{I}_1 - j125.7\mathbf{I}_2 = 0$$

$$(800 + j251.3)\mathbf{I}_1 - j125.7\mathbf{I}_2 = 6\angle 60^\circ$$

In right hand mesh

$$-j31.8\mathbf{I}_2 + 300\mathbf{I}_2 + 125.7\mathbf{I}_2 - j125.7\mathbf{I}_1 = 0$$

$$-j125.7\mathbf{I}_1 + (300 - j31.8 + j125.7)\mathbf{I}_2 = 0$$


$$\begin{bmatrix} (800 + j251.3) & -j125.7 \\ -j125.7 & (300 - j31.8 + j125.7) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 6\angle 60^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} 3. + j5.2 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} (800 + j251.3) & -j125.7 \\ -j125.7 & (300 + j93.8) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 6\angle 60^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} 3. + j5.2 \\ 0 \end{bmatrix}$$

$$\mathbf{v} = 300\mathbf{I}_2$$

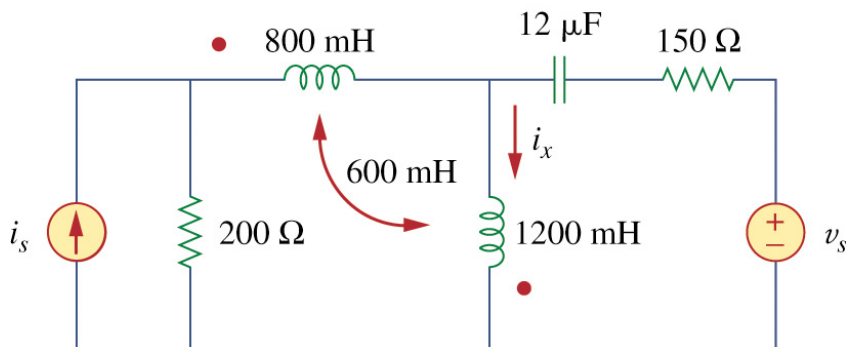**3:** Use mesh analysis to find  $i_x$  in the following circuit, when

$i_s = 4\cos(600t)$ ,  $v_s = 110\cos(600t + 30^\circ)$  Hint: Source transformation of the current source, after which the mesh current flows through both 800 mH and 1200 mH, inducing mutual inductance from each!



Convert the inductors and capacitors to reactances.

$$L_1 = 800\text{mH} = j600(0.8\text{H}) = j480\Omega$$

$$L_2 = 1200\text{mH} = j600(1.2\text{H}) = j720\Omega$$

$$M = 600\text{mH} = j600(0.6\text{H}) = j360\Omega$$

$$C = 12\mu\text{F} = \frac{1}{j600(1.2 \times 10^{-5}\text{F})} = -j139\Omega$$

$$\left( \text{note that } 600\text{mH} = M \leq \sqrt{L_1 L_2} = 980\text{mH} \right)$$

$$\text{Transform } i_s \text{ to } v_1 = i_s 200\Omega = 800 \cos(600t)$$

We are computing  $i_x$ , and have voltage sources, so mesh analysis is appropriate.

Assume  $i_1$  in the left mesh,  $i_2$  in the right, both flowing clockwise

The mutual inductance subtracts  $j\omega M i_1$  twice in the  $i_1$  mesh because  $i_1$  flows into the  $L_1$  dot and out of the  $L_2$  dot. But we *add* the mutual inductance effect of  $i_2$  because it flows into the  $L_2$  dot, inducing a positive voltage at the  $L_1$  dot. In the  $i_2$  mesh there is only the self inductance of the  $i_1$  current through the  $L_2$  inductor and the mutual effect of  $i_1$  in  $L_1$  on  $L_2$ .  $i_1$  flows into the  $L_1$  dot, inducing a positive voltage at the  $L_2$  dot.

Keeping these in mind, we can proceed by inspection


$$\begin{bmatrix} 200 + j480 + j720 - \underbrace{j360}_{L_1 \text{ effect on } L_2 \text{ due } i_1} - \underbrace{j360}_{L_2 \text{ effect on } L_1 \text{ due to } i_1} & -j720 + \underbrace{j360}_{L_2 \text{ effect on } L_1 \text{ due to } i_2} \\ -j720 + \underbrace{j360}_{L_1 \text{ effect on } L_2 \text{ due } i_1} & j720 - j139 + 150 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = - \begin{bmatrix} -800 \angle 0^\circ \\ 110 \angle 30^\circ \end{bmatrix}$$

$$\begin{bmatrix} 200 + j480 & -j360 \\ -j360 & 150. + j581 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 800 \\ -952.6 - j55 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1.2961 - j1.5643 \\ 0.8591 - j0.5835 \end{bmatrix}$$

$$i_x = i_1 - i_2 = 0.4370 - j0.9808 = 1.07 \angle -66^\circ$$

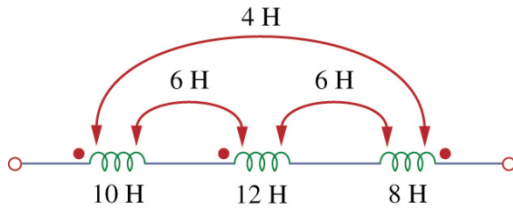4: Determine the inductance of the three series-connected inductors shown below.



Look at the total voltage across the 3 inductors.

$$v = \underbrace{j\omega L_1 I + j\omega L_2 I + j\omega L_3 I}_{\text{the self-inductance of the three inductors due to the common current, } I} + \underbrace{(+j\omega M_{12}I - j\omega M_{13}I)}_{\text{the effect of current } I \text{ flowing through the first inductor on the voltages at the other two inductors, using the "dot" conventions}} + \underbrace{(+j\omega M_{12}I - j\omega M_{23}I)}_{\text{the effect of current } I \text{ flowing through the second inductor on the voltages at the other two inductors, using the "dot" conventions}} + \underbrace{(-j\omega M_{13}I - j\omega M_{23}I)}_{\text{the effect of current } I \text{ flowing through the third inductor on the voltages at the other two inductors, using the "dot" conventions}}$$

Factoring the common  $j\omega$  factor and the common  $I$  factor from each term


$$v = j\omega LI, \text{ where } L = L_1 + L_2 + L_3 + 2M_{12} - 2M_{23} - 2M_{31} \\ = 10\text{H} + 12\text{H} + 8\text{H} + 2 \times 6\text{H} - 2 \times 6\text{H} - 2 \times 4\text{H}$$

$$\boxed{L=22\text{H}}$$

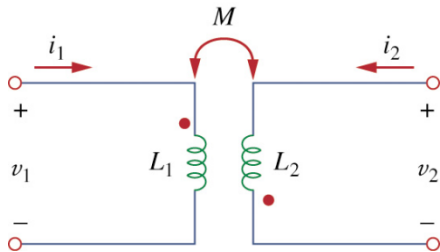5:

The coils shown below have  $L_1 = 40\text{mH}$ ,  $L_2 = 5\text{mH}$ , and  $k = 0.6$ . (Pay attention to the defined direction of the currents!) Find  $i_1(t)$ ,  $v_2(t)$  given that

$$v_1(t) = 10 \cos \omega t, i_2(t) = 2 \sin \omega t, \omega = 2000 \text{ rad/sec}$$



$$V_1 = i_1 \times j\omega L_1 - i_2 \times j\omega M$$

$$V_2 = i_2 \times j\omega L_2 - i_1 \times j\omega M$$

$$M = k\sqrt{L_1 L_2} = 0.6\sqrt{40 \times 10^{-3} \times 5 \times 10^{-3}} = 8.5 \text{ mH}$$

$$\text{From } V_1 \text{ equation above: } \frac{V_1 + i_2 \times j\omega M}{j\omega L_1} = i_1$$

$$i_1 = \frac{10 + (-j2)(j2000 \text{ r/s} \times 8.5 \times 10^{-3} \Omega\text{-sec})}{j(2000 \text{ r/s} \times 40 \times 10^{-3} \Omega\text{-sec})}$$

$$= -j0.55 = 0.55 \angle -90^\circ$$

$$i_1(t) = 0.55 \sin 2000t$$


From  $V_2$  equation,

$$V_2 = (-j2 \text{ A}) \times (j2000 \text{ r/s} \times 5 \times 10^{-3} \Omega\text{-sec}) - (-j0.55 \text{ A}) \times (j2000 \text{ r/s} \times 8.5 \times 10^{-3} \Omega\text{-s})$$

$$10.65 + j0$$

$$V_2(t) = 10.65 \cos 2000t$$

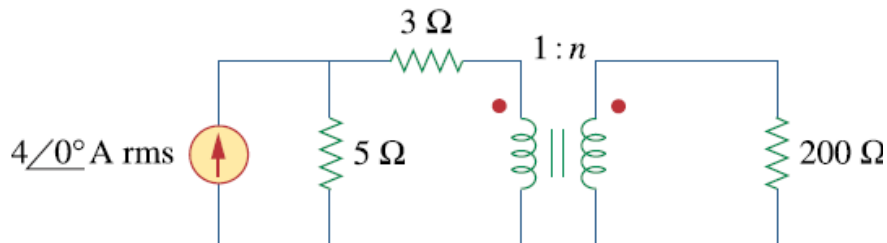**6:** Find  $n$  for the maximum power supplied to the 200 ohm load. Then determine the power to the 200 ohm load if  $n=10$ .



Transform the current source to get

$$v_s = 4 \times 5\Omega = 20\angle 0^\circ \text{ V.}$$

Reflect the  $200\Omega$  to the primary side:  $Z_{EQ} = \frac{Z}{n^2} = \frac{200\Omega}{n^2}$

With the voltage source transformation we have a voltage source and  $5+3\Omega$  in series. So the voltage source and series resistance represents the Thevenin equivalent of the left (primary) side.

For maximum power transfer,  $Z_L = Z_{TH}^* = 8\Omega = \frac{200\Omega}{n^2}$

$$n^2 = \frac{200}{8} = 25, n = 5.$$

If  $n = 10$  then the reflected impedance is  $\frac{200}{10^2} = 2\Omega$ .


The primary current is  $\frac{20\angle 0^\circ}{8\Omega + 2\Omega} = 2\angle 0^\circ \text{ A.}$

The voltage across the load is  $20\angle 0^\circ \times \frac{2\Omega}{8\Omega + 2\Omega} = 4\angle 0^\circ \text{ V}$

$$P = |\mathbf{V}_{RMS} \mathbf{I}_{RMS}^*| \cos(\theta_v - \theta_i) = 8 \cos(0) = 8 \text{ W}$$

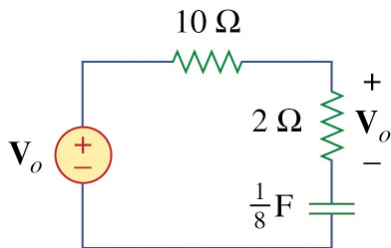7:

Obtain the transfer function  $\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}$  of the following circuit. **Note** that there is a "typo" in the circuit figure, and the voltage source should be labeled  $\mathbf{V}_i$ .



$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}$ . This is a series RLC circuit, and therefore a voltage divider.

$$\mathbf{H}(\omega) = \frac{2\Omega}{10 + 2 + \frac{1}{j\omega(1/8)}} = \frac{j2\omega/8}{1 + j10\omega/8} = \frac{j\omega/4}{1 + j\omega/0.8}$$